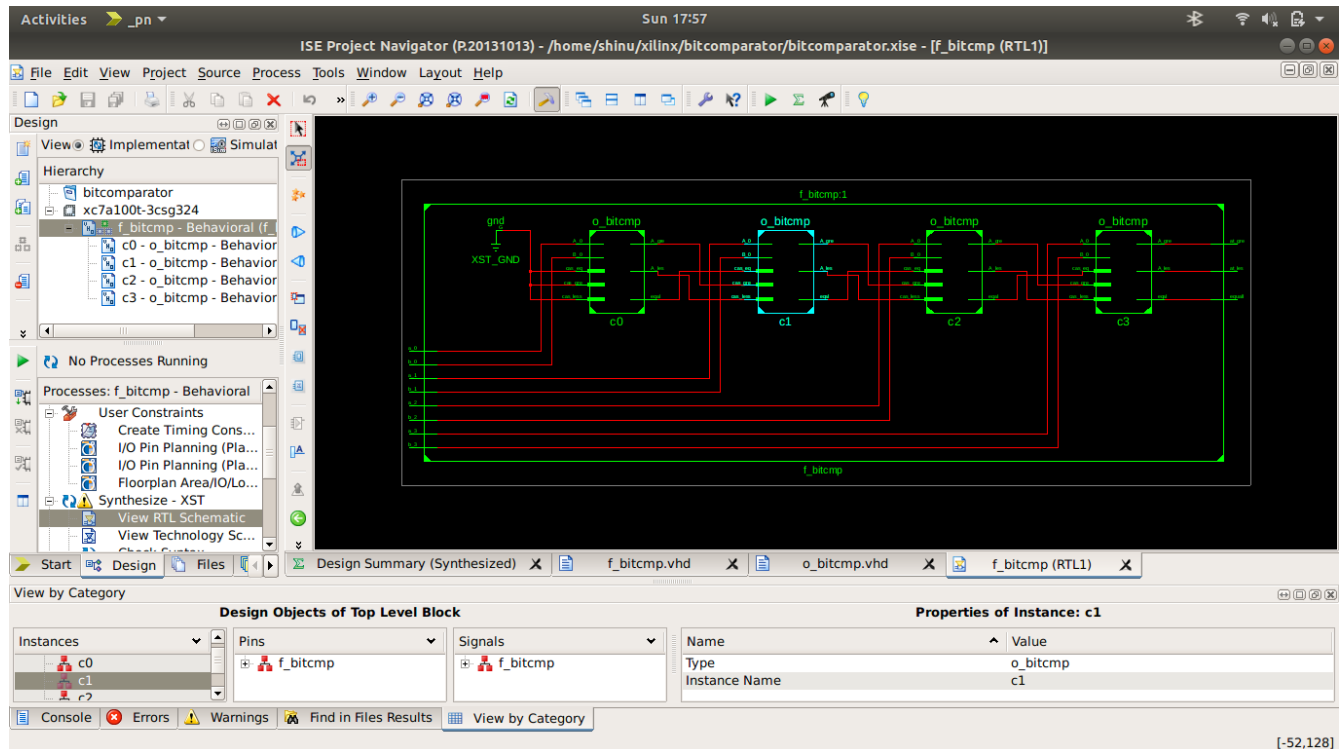


VHDL ASSIGNMENT

SHINU SHAJI C0761203


OBJECTIVE : DESIGN 4 BIT MAGNITUDE COMPARATOR USING STRUCTURAL APPROACH

SCHEMATICS :



[-52,128]

PULSE WAVE FORM :

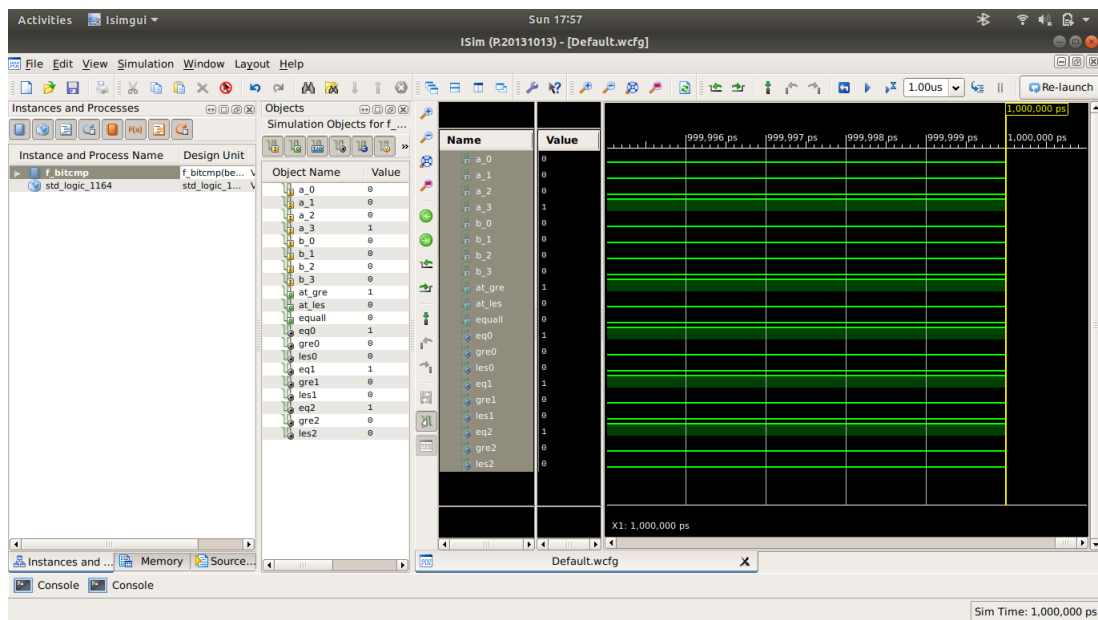

SOURCE CODE :

ONE BIT COMPARATOR :

```
-----
-- Company:
-- Engineer:
--
-- Create Date: 10:47:48 11/10/2019
-- Design Name:
-- Module Name: o_bitcmp - Behavioral
-- Project Name:
-- Target Devices:
-- Tool versions:
-- Description:
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
-----

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponentrtps.all;

entity o_bitcmp is
port(
A_0 : in std_logic;
B_0 : in std_logic;
A_gre : out std_logic;
eqal : out std_logic;
A_les : out std_logic;
cas_gre : in std_logic;
cas_eq : in std_logic;
cas_less : in std_logic
);

end o_bitcmp;
```

architecture Behavioral of o_bitcmp is

```
signal eq:std_logic ;
signal gre:std_logic ;
signal less:std_logic ;
signal test : std_logic;

begin

gre <= A_0 and not(B_0);
less <= not(A_0) and B_0 ;
eq <= (not(A_0) and not(B_0)) or (A_0 and B_0);
test <= cas_gre xor cas_eq xor cas_less;
process(eq,less,gre,cas_gre,cas_eq,cas_less)
begin

if eq = '1' and test ='1' then
    A_gre<=cas_gre;
    eqal<=cas_eq;
    A_les<=cas_less;
else
    A_gre<=gre;
    eqal<=eq;
    A_les<=less;

    end if;
end process;
end Behavioral;
```

4 BIT COMPARATOR :

```
-----
-- Company:
-- Engineer:
--
-- Create Date: 11:05:50 11/10/2019
-- Design Name:
-- Module Name: f_bitcmp - Behavioral
-- Project Name:
-- Target Devices:
-- Tool versions:
-- Description:
--
-- Dependencies:
--
```

```

-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
-----
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

```

```

entity f_bitcmp is
port(
    a_0 : in std_logic:= '0';
    a_1 : in std_logic:= '0';
    a_2 : in std_logic:= '0';
    a_3 : in std_logic:= '1';
    b_0 : in std_logic:= '0';
    b_1 : in std_logic:= '0';
    b_2 : in std_logic:= '0';
    b_3 : in std_logic:= '0';
    at_gre :out std_logic;
    at_les :out std_logic;
    equall :out std_logic
);
end f_bitcmp;

```

```

architecture Behavioral of f_bitcmp is
signal eq0 :std_logic;
signal gre0 : std_logic;
signal les0 : std_logic;
signal eq1 :std_logic;
signal gre1 : std_logic;
signal les1 : std_logic;
signal eq2 :std_logic;
signal gre2 : std_logic;
signal les2 : std_logic;
component o_bitcmp
port(
    A_0  : in std_logic;
    B_0  : in std_logic;
    cas_gre : in std_logic;
    cas_eq : in std_logic;

```

```
cas_less : in std_logic;  
A_gre : out std_logic;  
equal : out std_logic;  
A_les : out std_logic);
```

```
end component ;
```

```
begin  
c0:o_bitcmp port map (a_0,b_0,'0','0','0',gre0,eq0,les0);  
c1:o_bitcmp port map (a_1,b_1,gre0,eq0,les0,gre1,eq1,les1);  
c2:o_bitcmp port map (a_2,b_2,gre1,eq1,les1,gre2,eq2,les2);  
c3:o_bitcmp port map (a_3,b_3,gre2,eq2,les2,at_gre,equall,at_les);  
end Behavioral;
```